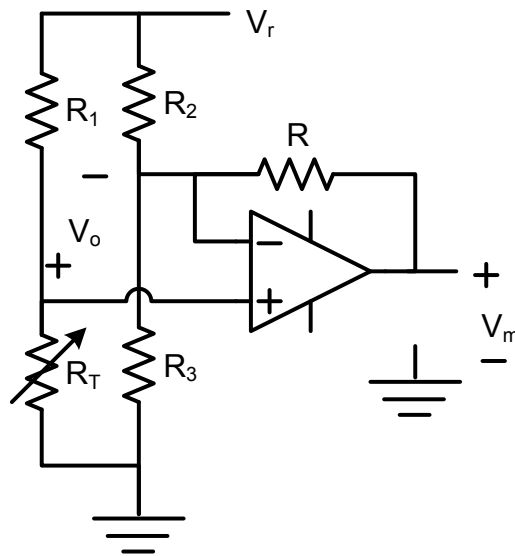



Wheatstone Bridge + OP

Due 6/12

Use the following circuit to measure temperature in the range from 0 °C to 100 °C, with a corresponding output (V_m) from 0V to 10V. The sensor (R_T) has the T.C.R. $0.075 \text{ } \Omega/K$, a resistance of $2000 \text{ } \Omega$ at 25 °C, and a maximum acceptable current of 1 mA. The OP is assumed to be ideal.

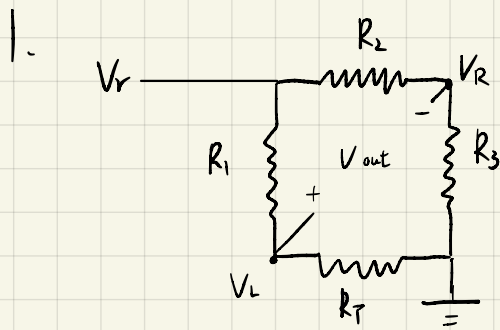
1. Without the OP and R , derive the equation for the output voltage V_o as function of V_r, R_1, R_2, R_3, R_T .
2. With the OP and R , derive the equation for the output voltage V_m as function of the other components.
3. Determine the value of each component (V_r, R_1, R_2, R_3, R) to satisfy the measurement requirements stated above.
4. Use Matlab to plot the output voltage (V_m , y-axis) as function of temperature measurand (x-axis).





$$V_L = V_r \cdot \frac{R_T}{R_1 + R_T} \quad V_R = V_r \cdot \frac{R_3}{R_2 + R_3}$$
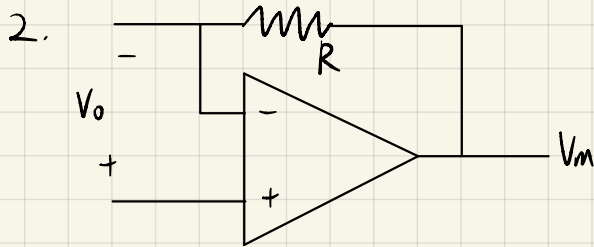
$$V_o = V_L - V_R = V_r \left(\frac{R_T}{R_1 + R_T} - \frac{R_3}{R_2 + R_3} \right) = V_r \left(\frac{R_T(R_2 + R_3) - R_3(R_1 + R_T)}{(R_1 + R_T)(R_2 + R_3)} \right)$$



$$V_m = V_o = V_r \left(\frac{R_2 R_T - R_1 R_3}{(R_1 + R_T)(R_2 + R_3)} \right)$$

voltage follower

3. $R_T = 2000$ $R_{Tf} = R_o (1 + \alpha \Delta T) = 2000 (1 + 0.075 \cdot 75) = 13250 \Omega \rightarrow \Delta R_T = 11250 \Omega$

$$I_{max} = 0.001 \text{ A} \rightarrow V_{max} = 13.25, \quad V_{L_{max}} = 13.25 \text{ V} \rightarrow V_R = 3.25 \text{ V}$$

$$\text{gain} = 0.5 \rightarrow V_r = 20 \text{ V}$$

$$3.25 = 20 \cdot \frac{R_3}{R_2 + R_3}, \quad R_3 = 13 \text{ k}\Omega, \quad R_2 = 67 \text{ k}\Omega$$

$$13.25 = 20 \cdot \frac{13250}{R_1 + 13250} \quad R_1 = 6750$$

$$R = 10 \text{ k}\Omega$$